
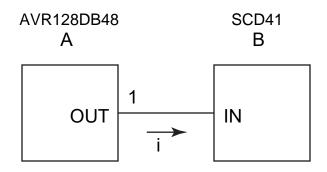
## Interface Checklist (revised 10/09/17) ESE280 Ken Short



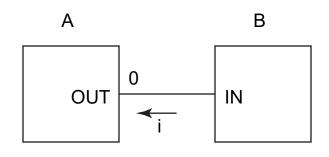


$$V_{OLmax(A)} < V_{ILmax(B)}$$

$$0.6 V < 0.99 V$$

$$I_{OLmax(A)} > I_{ILmax(B)}$$

$$10 \text{ mA} > 1 \text{ uA}$$

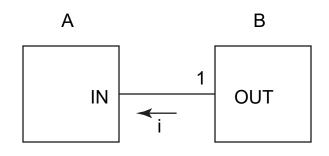


$$V_{\text{IHmin(A)}} < V_{\text{OHmin(B)}}$$

$$\underline{2.31 \text{ V}} < \underline{2.145 \text{ V}}$$

$$I_{\text{IHmax(A)}} < I_{\text{OHmax(B)}}$$
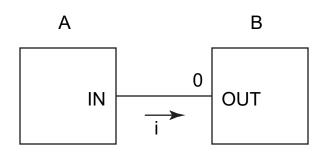
$$\underline{5 \text{ nA}} < \underline{330 \text{ uA}}$$



$$V_{\text{ILmax(A)}} > V_{\text{OLmax(B)}}$$

$$0.99 \text{ V} > 0.66 \text{ V}$$

$$I_{\text{ILmax(A)}} < I_{\text{OLmax(B)}}$$

$$5 \text{ nA} < 3 \text{ mA}$$